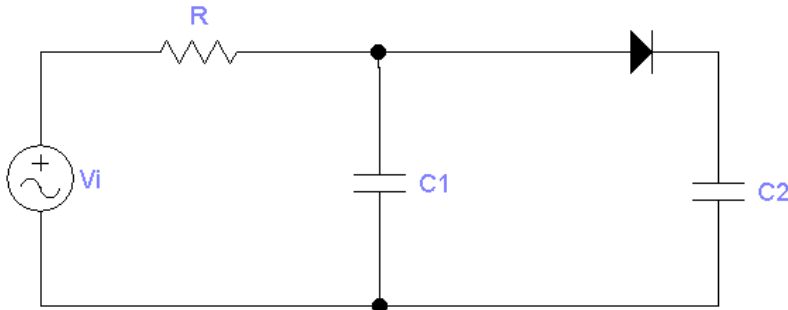


CENG 215 CIRCUITS and ELECTRONICS Project #2

Write a Python code to simulate the circuit below:



$$R = 1\Omega$$

$$C1 = 1F$$

$$C2 = 1F$$

Let your code perform the following functions:

Plot $V_1(t)$ and $V_2(t)$ of C1 (Capacitor 1) and C2(Capacitor 2) for two different $V_i(t)$ functions:

- a. $V_i(t) = 0.8$ volts
- b. $V_i(t) = 5 \sin(t)$ volts

At the end of the lab session, return a brief report (as Word or PDF document) that contains:

1. Python code.
2. Plots for two capacitor voltages.

NOTE: The Project will be studied as a teamwork, but the reports will be prepared and sent individually.